Sl. No.:

			1/.	19
egister	-			

2018

R

ELECTRICAL ENGINEERING (Degree Standard)

Time Allowed: 3 Hours

[Maximum Marks: 300

O PARTER

Read the following instructions carefully before you begin to answer the questions.

IMPORTANT INSTRUCTIONS

1. The applicant will be supplied with Question Booklet 15 minutes before commencement of the examination.

2. This Question Booklet contains 200 questions. Prior to attempting to answer the candidates are requested to check whether all the questions are there in series and ensure there are no blank pages in the question booklet. In case any defect in the Question Paper is noticed it shall be reported to the Invigilator within first 10 minutes and get it replaced with a complete Question Booklet. If any defect is noticed in the Question Booklet after the commencement of examination it will not be replaced.

3. Answer all questions. All questions carry equal marks.

4. You must write your Register Number in the space provided on the top right side of this page. Do not write anything else on the Question Booklet.


5. An answer sheet will be supplied to you, separately by the Room Invigilator to mark the answers.

6. You will also encode your Question Booklet Number with Blue or Black ink Ball point pen in the space provided on the side 2 of the Answer Sheet. If you do not encode properly or fail to encode the above information, action will be taken as per commission's notification.

7. Each question comprises four responses (A), (B), (C) and (D). You are to select ONLY ONE correct response and mark in your Answer Sheet. In case you feel that there are more than one correct response, mark the response which you consider the best. In any case, choose ONLY ONE response for each question. Your total marks will depend on the number of correct responses marked by you in the

Answer Sheet.

 8. In the Answer Sheet there are four circles (A), (B), (C) and (D) against each question. To answer the questions you are to mark with Blue or Black ink Ball point pen ONLY ONE circle of your choice for each question. Select one response for each question in the Question Booklet and mark in the Answer Sheet. If you mark more than one answer for one question, the answer will be treated as wrong. e.g. If for any item, (B) is the correct answer, you have to mark as follows:



- 9. You should not remove or tear off any sheet from this Question Booklet. You are not allowed to take this Question Booklet and the Answer Sheet out of the Examination Hall during the time of examination. After the examination is concluded, you must hand over your Answer Sheet to the Invigilator. You are allowed to take the Question Booklet with you only after the Examination is over.
- 10. The sheet before the last page of the Question Booklet can be used for Rough Work.

11. Do not tick-mark or mark the answers in the Question Booklet.

- 12. Applicants have to write and shade the total number of answer fields left blank on the boxes provided at side 2 of OMR Answer Sheet. An extra time of 5 minutes will be given to specify the number of answer fields left blank.
- 13. Failure to comply with any of the above instructions will render you liable to such action or penalty as the Commission may decide at their discretion.

20003138

CEEE/18 2


- 1. When two 2-port network are connected in parallel, it is convenient to use
 - Open circuit impedance parameters
- (B) Short circuit impedance parameters


(C) Z parameters

- (D) Y parameters
- In a RLC series circuit, the impedance at resonance is 2.
 - (A) Zero


Infinity

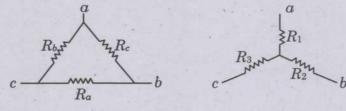- (D) $\frac{L}{CR}$
- In fig. 1 R_a , R_b and R_c are 20 Ω , 10 Ω and 10 Ω respectively. The resistances R_1 , R_2 and 3. R_3 in Ω of an equivalent star-connection are



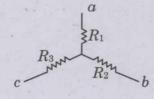


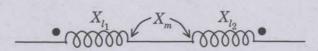- (1) 2.5, 5, 5
- (B) 5, 2.5, 5 (C) 5, 5, 2.5
- (D) 2.5, 5, 2.5
- The equivalent inductance of two coils A and B connected as in the figure given below. 4.



 $(A) \quad X_{l_1} + X_{l_2} - 2X_m$

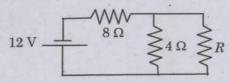- (B) $X_{l_1} + X_{l_2} + X_m$ (D) $X_{l_1} + X_{l_2} + 2X_m$
- What shall be the value of R, if it has to absorb maximum power from source? 5.



=


- (C) 4Ω
- (D) 8Ω


- Which of the following theorems is a manifestation of the law of conservation of energy? 6.
 - Reciprocity theorem

(B) Thevenin's theorem

Tellegen's theorem

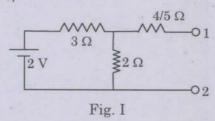- (D) Norton's theorem
- 7. The Norton's equivalent circuit shown in the figure II is drawn from figure I. The value of I_{SC} and R_{eq} in the fig. II is



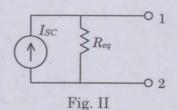

- 5/2 A and 2Ω (A)
- (C) 4/5 A and 12/5 Ω

- 2/5 A and 1 Ω
- 2/5 A and 2 A

8. Match List I with List II.

> List I (Condition)

List II

(Transient response)

(a) R = 0

- Undamped oscillations 1.
- $R < 2\sqrt{L/C}$ (b)
- 2. Damped oscillations
- $R = 2\sqrt{L/C}$ (c)
- 3. Critically damped response
- $R > 2\sqrt{L/C}$ (d)
- 4. Non-oscillatory response
- (c) (d) 3
- (B) 3 4
- 2 (C) 3 1
- (D) 1 2
- In a RLC series circuit, $R = 8 \Omega$, L = 4 H, $C = \frac{1}{4} F$. The natural response is 9.
 - (A) over damped

(B) under damped

critically damped

- (D) oscillatory
- The characteristics impedance of lossless transmission line is given by 10.
 - $\sqrt{C/L}$ (A)
- (B) \sqrt{LC}
- (D) $1/\sqrt{LC}$

- 11. Image theory is applicable to problem involving
 - Electro static field only
 - Magneto static field only (B)
 - Both electro static and magneto static fields (C)
 - Neither electro static nor magneto static fields (D)
- The relation between electric intensity E, voltage applied V and the distance between the 12. plates of a parallel plate capacitor is
 - (A) E = V/d

- (B) $E = V \times d$ (C) $E = V/d^2$ (D) $E = V \times d^2$
- Which one of the following is true for the value of capacitance between two spheres, whose 13. separation is very much larger than their radii R?
- $2\pi \in_0 R \qquad \text{(C)} \quad \frac{2\pi \in_0}{R} \qquad \text{(D)} \quad \frac{4\pi \in_0}{R}$
- The inductance of a solenoid of 10 turns is 5 µH. Which one of the following is correct value 14. of inductance when the number of turns is 20 and length is doubled?
 - (A) 10 uH
- (B) 20 uH
- 5 uH

- Consider the following three equations: 15.
 - $\nabla \times \overrightarrow{E} = -\frac{\partial \overrightarrow{B}}{\partial t}$
 - 2. $\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t}$
 - $\nabla \times \overrightarrow{B} = 0$ 3.

Which of the above are Maxwell's equations?

1, 2 and 3

(B) 1 and 2 only

2 and 3 only (C)

1 and 3 only.

- 16. The expression $A + (B \cdot C)$
 - (A) $A \cdot B + C$

 $A \cdot B + A \cdot C$

(C)

 $(A+B)\cdot (A+C)$

17.	To re	educe temperature error in shunted	lamn	neter, swamping	resistance	is	connected
	(A)	in series with the shunt					
	(B)	in parallel with the shunt					
	9	in series with the meter					
	(D)	in between shunt and the meter					
18.	The p	rinciple of voltage to time conversion i	s used	Lin			
	40	Dual slope type DVM					
8	(B)	Successive approximation type DVM					
	(C)	Integrating type DVM					
	(D)	Continuous balance DVM					
19.	The t	urn off time of a LCD is in the order of					
	(A)	18	(B)	1 mS			
	405	10 mS	(D)	10 nS			
20.	, An os	cilloscope indicates					
	(A)	RMS value	(B)	Average value			
	45	Peak to peak value	(D)	DC value			
21.	Schm	itt trigger used in digital measuremen	t of ti	me converts the in	put into		
	(A)	Square wave	(B)	Sine wave			
	w	Pulses	(D)	Sawtooth wave			
22.	The g	auge factor in a strain gauge is defin	ned as	(L - length, D -	diameter. H	2 - 1	resistivity
		sistivity)					, ,
	(A)	$\Delta L/L$		$\Delta R/R$			
		$\Delta R/R$	10)	$\Delta L/L$			
	(C)	$\frac{\Delta R/R}{\Delta D/D}$	(D)	$\frac{\Delta R/R}{\Delta \alpha/\alpha}$			
		LL I L		ΔρΙρ			

23.	Harmonic	distortion	io	dua	to
40.	Harmonic	distortion	12	uue	U

- (A) Linear-behaviour of the circuit elements
- Non linear behaviour of the circuit elements
- (C) Change in behaviour of circuit elements due to temperature
- (D) Due to circuit resistance

24. A Varmeter is used to indicate the

(A) overloads

(B) out of phase

reactive power

(D) real power

25. In two wattmeter method of measuring 3-phase power factor is 0.5, then one wattmeter will read

(A) $\frac{w}{2}$

(B) zero

(C) $\sqrt{2}w$

(D) $\frac{w}{\sqrt{3}}$

26. Moving iron instruments are

(A) Attraction type

- (B) Repulsion type
- Attraction and repulsion type
- (D) Dynamometer type

27. If σ is standard deviation, variance is

(A) $\sqrt{\sigma-1}$

(B) $(\sigma)^{1.5}$

(C) \ \ \sigma^2

(D) $(\sigma)^{1/2}$

28. Calculate the sensitivity of a $200 \,\mu A$ meter movement which is to be used as a dc voltmeter.

(A) 5000 KΩ/V

(B) 500 KΩ/V

(C) 50 KΩ/V

5 KΩ/V

29. Which of the following statements is not necessarily correct for open control system?

- (A) Input command is the sole factor responsible for providing the control action
- Presence of non-linearities causes malfunctioning
 - (C) Less expensive
 - (D) Generally free from problems of non-linearities

- 30. Which of the following is a reason to employ negative feedback in most automatic control systems?
 - (A) $G_C < G$

- (B), $G_C > G$
- It results in stable output
- (D) It results in unstable output
- The loop gain GH of a closed loop systems is given by the expression $\frac{K}{s(s+2)(s+4)}$ the value of K for which the system just becomes unstable is
 - (A) K = 6

(B) K = 8

(C) K = 48

- (D) K = 96
- 32. The Asymptotes in the root locus plot of unit feed back configuration of $G(s) = \frac{1}{s(s+1)(s+2)}$ intersect with the real axis at
 - (A) -1.25

€ −1.5


(C) -1

- (D) -1.15
- 33. Which of the following is the full form of SISO?
 - Single input single output
- (B) Sustained input sustained output
- (C) Steady input steady output
- (D) Sequential input sequential output
- 34. A unity feedback system having open loop gain $G(s)1+(s)=\frac{k(1-s)}{(1+s)}$ becomes stable when
 - $(A) \qquad |k| > 1$
- (B) k > 1
- |k| < 1
- (D) k < -1
- 35. The first two rows of Routh's tabulation of a third order equation are as follows:

This means there are

- (A) Two roots at $s = \pm j$ and one root in right half s plane
- (B) Two roots at $s = \pm j2$ and one root in left half of s plane
- (C) Two roots at $s = \pm j2$ and one root in right half of s plane
- Two roots at $s = \pm j$ and one root in left half of s plane

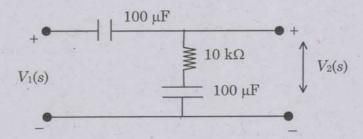- 36. Which of the following does not define a transfer function of a closed loop control system?
 - (A) It is a ratio of actual output to the referred output
 - It is a ratio of actual output to the actual input
 - (C) It has magnitude only
 - (D) It has phase only
- 37. The transfer function $\frac{V_2(s)}{V_1(s)}$ of the circuit shown in Fig. is



- (A) $\frac{0.5 s + 1}{s + 1}$
 - $rac{s+1}{s+1}$ (B) $rac{s}{s+1}$
- (C) $\frac{s+2}{s+1}$

- $\frac{s+1}{s+2}$
- 38. How can the reactive power delivered by a synchronous generator be controlled?
 - (A) By changing the prime mover input
 - By changing the excitation
 - (C) By changing the direction of rotation
 - (D) By changing the prime mover speed
- 39. With the load power factor of unity, the effect of armature reaction on the main field flux of an alternator is
 - (A) Distortional

(B) Magnetizing

(C) Demagnetizing

- (D) Nominal
- 40. In the 'V' curve of a synchronous motor, the 'x' axis parameter and 'y' axis parameter are respectively.
 - (A) Armature current and field current
- (B) Power factor and field current
- (C) Armature current and torque
- Field current and armature current

41.				rotor reactance per phase that is four times h the maximum torque developed is
	(A)	1500 rpm		1125 rpm
	(C)	1000 rpm	(D)	3000 rpm
42.	In ar	n induction motor if the air gap is	increased	
	(A)	speed will reduce	(B)	efficiency will improve
	(0)	power factor will be lowered	(D)	breakdown torque will reduce
43.	In ar	n induction motor, what is the rati	o of the rot	or copper loss and rotor input?
	(A)	$\frac{1}{s}$	(8)	s
	(C)	1-8	(D)	$\frac{s}{1-s}$
44.	impe	dances of 4 and 2 are operating ir percent.	parallel. T	and voltage ratios but unequal percentage Transformer A will be running over-load by
	(A)	50	(B)	66
	Way-	33	(D)	25
45.	The	voltage applied to the h.v. side o		rmer during short-circuit test is 2% of its - percent of the rated core loss.
	(A)	4	(B)	
	(C)	0.25	O)	0.04
46.	Whice	h three phase connection can be u etween its output and correspondi	sed in a tra	nsformer to introduce a phase difference of ne voltages?
	W	Star-Delta	(B)	Star-Star
	(C)	Delta-Delta	(D)	Delta-Zigzag
47.	What	t is the load at which maximum ef loss of 1 kW and full load copper lo	ficiency occ oss of 2 kW	curs in case of a 100 kVA transformer with
	(A)	100 kVA	(B)	70.7 kVA
	(C)	50.5 kVA		25.2 kVA
CEE	E/18		10	

- Surge impedance is given by 48.

 \sqrt{yz} (C)

- circuit breakers are for low and medium voltages. 49.
 - A.C. air break

(B) Air blast

SF6

- Vacuum (D)
- Flux linkages within a conductor producing flux in Wb-T/m are given by 50.
 - (A) 0.5×10^{-7}

(C) $\frac{\mu}{4\pi}$

- (D) $\frac{\mu I}{4\pi}$
- With usual notation, the sag d is given by 51.
 - (A) $d = H \cosh \frac{wl}{H}$

(B) $d = \frac{wl}{2T^2}$

- (C) $d = \frac{H}{W} \left[\cosh\left(\frac{wl}{H}\right) + 1 \right]$
- $d = \frac{H}{W} \left[\cosh \left(\frac{wl}{H} \right) 1 \right]$
- Match List I with List II and select the correct answer using the codes given below the lists. 52.

List I

List II

- Thyrite arrester (a)
- Tower location 1.
- Sag template (b)
- 2. Cross bonding
- Cable sheaths (c)
- Restriking voltage 3.
- Circuit breaker (d)
- Non-linear resistor 4.

- (a)
- (b)
- (c)

(d)

2

3

- (A)
- 3

- 3
- (D)

- 2

53.	The	current chopping tendency is minimi	sed by using the SF6 gas at relative	ely
	(A)	high pressure and low velocity		
	(B)	high pressure and high velocity		
	(C)	low pressure and low velocity		
	(D)	low pressure and high velocity		
54.	Prote	section scheme used for detection of ing power into a grid employs	loss of excitation of a very large	generating unit
	(A)	under voltage relay		
	(B)	offset mho relay		
	(C)	under frequency relay		
	(D)	percentage differential relay		
55.	The e	expression $AB + A\overline{B}$		
	(A)	В	A .	
	(C)	1	(D) 0	
56.	Thor	voltages at the two and a f - 1:	10011	
00.	of the	voltages at the two ends of a line are line is	132 kV and its reactance is 40 ohr	ns. The capacity
	VA	435.6 MW		
	(B)	217.5 MW		
	(C)	251.5 MW		
	(D)	500 MW		
57.	Four	identical alternators each rated for are working in parallel. The short cir	20 MVA, 11 kV having a sub-transicuit level of the bus-bars is	ent reactance of
	W	500 MVA		
	(B)	400 MVA -		
	(C)	125 MVA		
	(D)	80 MVA		
CEE	TE/10			
CEE	E/18	TOTAL PROPERTY OF THE PARTY OF	12	=

- 58. By placing an inverter between both inputs of an S-R flip flop, the resulting is a
 - (A) S-R latch

(B) T-flip flop

(C) J-K flip flop

D- flip flop

59. Given: X = 1010100

Y = 1000011

Perform subtraction using 1's complement X - Y = ?

(A) 0001001

(B) 1001001

0010001

- (D) 0010101
- 60. Simplify the following Boolean expression to a minimum number of literals.

xy + x'z + yz

xy + x'z

(B) xy + yz

(C) x'z + yz

- (D) x'y + yz
- 61. In a two stage amplifier, if the two stages has voltage gains as 20 dB and 40 dB, then the overall voltage gain in dB is
 - (A) 60 dB

(B) 800 dB

(C) 20 dB

- (D) 10 dB
- 62. A transistor used as a switch is operated in
 - (A) active region

(B) saturation region

(C) cut off region

- cut off and saturation region
- 63. In a CE transistor β may be expressed in terms of α as
 - (A) $\beta = \frac{1-\alpha}{\alpha}$

(B) $\beta = \frac{1+\alpha}{\alpha}$

(C) $\beta = \frac{\alpha}{1+\alpha}$

 $\beta = \frac{\alpha}{1-\alpha}$

64. The frequency of oscillation of RC phase shift oscillator using OP-AMP is

(A)
$$f_0 = \frac{1}{2\pi RC}$$

$$f_0 = \frac{1}{2\pi RC\sqrt{6}}$$

(C)
$$f_0 = \frac{1}{4\pi RC}$$

$$\text{(D)} \quad f_0 = \frac{1}{4\pi RC\sqrt{6}}$$

65. The contents of a four bit register are initially 1011. The register is shifted 3 times to the right with the serial input being 101111. What are the contents of the register after the final shift?

(A) 1101

(3) 1111

(C) 1110

(D) 1011

66. An 8-input multiplexer is to be builts with a tree network of 2-input multiplexers. The number of 2-input multiplexers required are

(A) 2

(8) 4

(C) 8

(D) 16

67. A four bit counter has a maximum modulus of


(A) 4

(B) 6

(C) 8

(16)

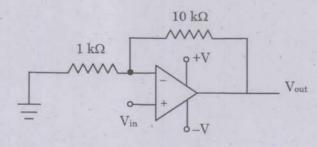68. For the non inverting amplifier shown, find the output voltage for a input of one volt.



(A) 1 volt

(B) 10 volt

(6) 11 volt

(D) 0.1 volt

- 69. For a 6 pulse converter, the intervals between firing of six SCRs is
 - (A) 90°

(B) 45°

(C) 30°

- 60°
- 70. If V_{ph} is the rms value of line to neutral voltage applied to three phase full converter, then the maximum value of the output voltage is given by
 - (A) $3\sqrt{2} V_{ph} / \pi$

(B) $3\sqrt{3} V_{ph}/\pi$

 $3\sqrt{6} V_{ph} / \pi$

- (D) $6\sqrt{3} V_{ph}/\pi$
- 71. Which of the following circuit cannot be operated directly from the mains?
 - (A) Bridge rectifier

(B) Centre-tap rectifier


(C) Half wave rectifier

- (D) Voltage doubles
- 72. For a full wave single phase rectifier with freewheeling diode, the width of the freewheeling diode current pulse for each 2π cycle is
 - (A) $\pi + \alpha$

(B) $\pi - \alpha$

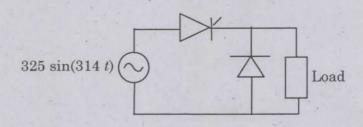(C) π

- D 2α
- 73. The figure shows the circuit diagram of a rectifier. The load consists of a 10 Ω resistance and an inductances 0.05 H connected in series. Assuming ideal thyristor and diode, the firing angle in degree to obtain an average load voltage of 70 V is




(A) 79.3°

(B) 69.3°

(C) 90°

(D) 108.3°

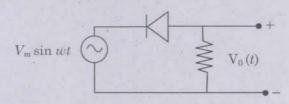74. In the following circuit the average value of $V_0(t)$ will be



- (A) 0
- (C) $V_m/\sqrt{2}$

- $\frac{-V_m}{\pi}$
- (D) -V_m

75. An electric motor developing a starting torque of 15 Nm starts with a load torque of 7 Nm on its shaft. If the acceleration at start is 2 rad/sec², the moment of inertia of the system must be

- (A) 0.25 Kgm²
- 4 Kgm²

- (B) 0.25 Nm²
- (D) 4 Nm²

76. Match:

List I

List II

(Circuit)

(Type of conversion)

- (a) Controlled Rectifier
- 1. Fixed DC to variable voltage, variable frequency AC
- (b) Chopper
- 2. Fixed DC to variable DC
- (c) Inverter
- 3. Fixed AC to variable DC
- (d) Cyclo converter
- 4. Fixed AC to variable frequency AC
- (a) (b) (c) (d) (A) 2 3 1 4 (B) 3 2 4 1 (C) 2 3 4 1
- 3 2 1 4

77. The most suitable device for high frequency inversion in SMPS is

(A) BJT

(B) IGBT

MOSFET

(D) GTO

- 78. If the clock frequency is 5 MHz, how much time is required to execute an instruction of 18 T-states?
 - 3.6 micro seconds

(B) 3.6 milli seconds

(C) 0.36 milli seconds

- (D) 0.036 micro seconds
- 79. The instruction IMUL DH in 8086 results in
 - (A) AL multiplied by DH and the unsigned product is in AX
 - AL multiplied by DH and the signed product is in AX
 - (C) AL multiplied by DH and the unsigned product is in AL
 - (D) AL multiplied by DH and the unsigned product is in AH
- 80. Specify the memory location and its contents after the following instructions are executed in 8085

MVI B, F7 H

MOV A, B

STA XX75 H

HLT

- (A) Location: 2075 H, Content: 7F H
- Location: 2075 H, Content: F 7H
- (C) Location: 2075 H, Content: 00 H
- (D) Location: 2075 H, Content: 07 H
- 81. In radix 2 DIT, Fast Fourier Transform computation the number of additions and multiplications are given by
 - (A) N(N-1) and N^2 respectively
 - $N\log_2 N$ and $\frac{N}{2}\log_2 N$ respectively
 - (C) N^2 and $N \log_2 N$ respectively
 - (D) $\frac{N}{2}\log_2 N$ and N(N-1) respectively
- 82. The filter that has a monotonic pass band and an equiripple stop band is
 - Type II Chebyshev filter
- (B) Type I Chebyshev filter

(C) Elliptic

(D) Butterworth

	(D)		p to loca mulator		if the LSF	3 of accur	mulator is LOW and also	sets the	LSB of	
85.	Mate	ch List	I with I	ist II an	d select the	e answer :				
			List I				List II			
	(a)		Detection of Periodic signal in noise				Increase in Bandwidth			
	(b)	Recov	very of ba	and		2.	Slope overload error			
				e from it						
	(c)			npled va ation of		9	Nyawiat wata			
	(d)		modula		signais	3. 4.	Nyquist rate Cross correllation			
	(a)	Dena	modula	.01011		4.	Cross correlation			
		(a)	(b)	(c)	(d)					
	(A)	4	3	1	2					
	(B)	3	4	2	1					
	(C)	4	3	2	1 .					
	(D)	4	2	1	3					
86.	Con	sider t	he follow	ing drav	vbacks:					
	1.	Slop	e over lo	ad noise	THE RESERVE OF THE PERSON OF T					
	2.	Serr	ation no	ise						
	3.	Gra	nular no	ise						
4	4.	Qua	ntization	n noise						
	Whi	ch of th	hese dra	wbacks	does Delta	modulatio	n have?			
	(A)	1 an	id 2			(B) 1 and 4			
	405	1 an	id 3			(D				
					- 1714					
CEE	E/18					18			±	11

Data transfer completion

Modulo 128 mark

jump to location X if the LSB of accumulator is HIGH and also clears the LSB of

A high on TC line in 8257 indicates

Byte transferred is 1

No data transferred

accumulator

The 8051 instruction JBC ACC.O, X makes the program to

jump to location X if the LSB of accumulator is HIGH

jump to location X if the LSB of accumulator is LOW

83.

84.

(C)

(A)

(C)

	(A)	$\sin \theta$	(B)	$\cos \theta$
	(C)	$1/\sin\theta$	1	$1/\cos\theta$
88.	The s	surface temperature of the sun is appro	oximat	ely
	W	6000° K	(B)	80,000° C
	(C)	100,000° F	(D)	10,00,000° K
89.	The a	perture area of a solar module is defin	ned as	
	(A)	the total area of the solar module		
	AN .	the area of PV – active parts only		
	(C)	the total area less the PV - active are	ea	
	(D)	the sum of the module area and the I	PV – ad	ctive area
90.	Instr	ument used to measure the total hemi-	spheric	cal solar radiation
	(A)	Pyrheliometer	(B)	Pyranometer
	(C)	Anemometer	(D)	Sunshine Recorder
91.	Trick	le charging of a storage battery helps	to	
	(A)	Maintain proper electrolyte level	(B)	Increase its reserve capacity
	(C)	Prevent sulphation	VD)	Keep it fresh and fully charged
92.	The b	est indication about the state of charg	ge on a	lead acid battery is given by
	(A)	output voltage		
	(B)	temperature of electrolyte		
	401	specific gravity of electrolyte		
	-(D)	colour of the electrolyte		
93.	For a	battery, A C-rate of 'n' indicates that	the ba	ttery fully discharges in
	(A)	n hours	(B)	$C \times n$ hours
	(C)	C/n hours	0	1/n hours

When the sun is at an angle θ with the zenith, the air mass AM is given by?

87.

94. Find the voltage across AB in the circuit shown in fig. 1.


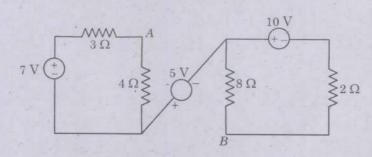


Fig. 1

(A)

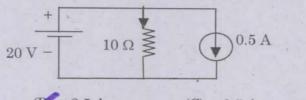

Current through the voltage source in the following circuit is 95.



(A) 2 A



A dc voltage V is applied at time t = 0 to a series RC circuit. The steady state current is 96.

(A)
$$\frac{V}{R}$$

(B)
$$\frac{V}{C}$$

(B)
$$\frac{V}{C}$$
 (D) $\frac{V}{\sqrt{R^2 + C^2}}$

A 100 watt electric bulb draws current I amp from 200 volt, 50 Hz supply. The current I is 97.

(B)
$$\sqrt{2}$$
 A

(C)
$$\frac{1}{\sqrt{2}}$$
 A

A series connected load draws a current $i(t) = 4\cos(100\pi t + 10)A$ with the source of 98. $V(t) = 120\cos(100\pi t - 20) \text{ V}$. The apparent power and PF are

(A) 480 VA, 0.8 leading

(B) 480 VA, 0.8 lagging

240 VA, 0.8 leading

(D) 240 VA, 0.8 lagging

99. Superposition theorem is not applicable for

(A) Voltage calculations (B) Bilateral elements

Power calculations

(D) Passive elements


- 100. The code where all successive numbers differ from their preceding number by single bit is
 - (A) Binary code

(B) BCD code

(C) Excess-3 code


- Gray code
- 101. At resonant frequency, a RLC series circuit draws maximum current due to
 - the difference between capacitive reactance and inductive reactance is zero
 - (B) the impedance is more than its resistance
 - (C) the voltage across capacitor is equal to the applied voltage
 - (D) the PF is less than unity
- 102. Two coils X of 1000 turns and Y of 2000 turns are placed such that 60% of the flux produced by coil X links coil Y. A current 1 A in coil X produces 0.1 MWb flux. The mutual inductance between the coil is
 - 0.12 H
- (B) 0.08 H
- (C) 0.06 H
- (D) 0.04 H

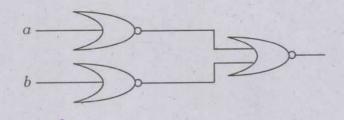103. The logic performance of the following circuit is



- (A) NAND
- (P) ANI
- C) NOT
- (D) OR

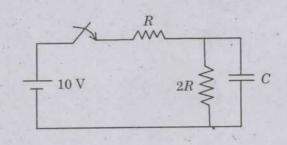104. The time constant of the network shown in figure is



- (A) 2 RC
- (B) 3RC
- (C) RC/2
- (B) 2RC/3

100.	The relati	ousnip betw	een ei	ectric field and	electri	c potential is g	iven by		
	(A) \overline{E}	$=-\nabla^2 V$	(B)	$\overline{E} = V$	50	$\overline{E} = -\nabla V$	(D)	$\overline{E} = -\frac{\nabla}{2}$	<u>V</u> 2
106.	The expre	ession for lift	ing po	wer of an electr	romagi	net is			
	(A) F =	= BH	(B)	F = 2BH	(C)	$F = BH^2$	0	$F = \frac{1}{2}B$	$^{\circ}H$
107.	the force I	per metre of	eacn c	s carry 100 A. I	currer	nt flow is in opp	osite dir	d by 20 rection?	nm, what is
	0.1	N/m	(B)	0.2 N/m	(C)	10 N/m	(D)	20 N/m	
108.	Current fl	ow in dielect	tric is						
		duction curr			(B)	current does	not flow	in dielec	tric -
	disp	olacement cu	irrent		(D)	free charge cu	irrent		
109. 110.	(A) 2 A	/m	O)	carries a curr 1 A/m e forces experie	(C)	10 A/m	(D)	4 A/m	
	(A) Cou	lomb's law				Newton's law		Halis	
	· Am	pere's law			(D)	Gauss law			
111.	electric fie	Id at $P(1, 1, 1)$	1) m?	$f \sigma = 2 \text{ c/m}^2 \text{ is}$			lane. W	hat is tl	ne value of
	1.1	× 10 ⁺¹¹	(B)	2.2×10^{-11}	(C)	3.3	(D)	0	
112.	nux densit	y D is given	by	experienced by					
	(A) $F =$	$Qv \times B$	(B)	$F = B(Q \times v)$	(C)	$F = B(v \times \tilde{Q})$	(D)	B = F(v)	× B)
13.			100000	ing sphere is	(C)	minimum	(D)	maximu	m

114.	Which of the following amplifier has highest efficiency?	
	(A) Class-A (B) Class-B (C) Class-C (D) Class-AB	
115.	What is the capacitance of a capacitor having a stored energy of 10 microjoules with a applied voltage of 5 volts?	n
	(A) $C = 0.4 \ \mu\text{F}$ (C) $C = 0.12 \ \mu\text{F}$ (D) $C = 1 \ \mu\text{F}$	
116.	A point charge of $4\pi\varepsilon_0 C$ is situated at origin. What is the value of field intensity at	t
	(0, 0, 1) m? (A) 1 V/m (B) 2 V/m (C) 4 V/m (D) 0 V/m	
117.	A parallel plate capacitor filled with two dielectrics is shown in the figure below. If the electric field in the region A is 4 kV/cm , the electric field in the region B in kV/cm is	e
	- V/2 / 1 2	
	$A \qquad B \qquad 2 \text{ cm}$ $\in_r = 1 \in_r = 4$	
	$\epsilon_r = 1 \epsilon_r = 4$	
	(A) 1 (B) 2 (D) 16	
	(A) 1 (b) 2	
118.	Inductance is measured by	
	(A) Wien bridge (B) Schering bridge	
	Maxwell's bridge (D) De Sauty's bridge	

119. A basic D'Arsonval movement with a full scale deflection of 50 μA and internal resistance of 500 Ω is used as a volt meter. Determine the value of multiplier resistor to measure a voltage range of 0–10 V.

(A) 2.5 K Ohms

P) 199.5 kΩ

(C) 400 Ω

(D) 200 Ω

120. When a galvanometer is connected in series with high resistance it becomes,

(A) an ammeter

a voltmeter

(C) a wattmeter

(D) a multimeter

		List	1			List 2	
		(Tern	ns)			(Meanings)	
	(a)	Preci	sion		1.	The smallest detected	change in the input quantity which can be
	(b)	Accur	racy ·		2.	Closeness of t	the reading to true value
	(c)	Resol	lution		3.	Measure of re	eproducibility
	(d)	Statio	c sensitiv	vity	4.	Ratio of infin change in inp	itesimal change in output to infinitesima ut
		(a)	(b)	(c)	(d)		
	(A)	2	3	1	4		
	(B)	3	2	4	1		
	VOT	3	. 2	1	4		
	(D)	2	3	4	1		
122.	Whic	ch one	of the fo	llowing n	nateria	ls is not used a	s a piezoelectric transducer?
	(A)		nelle salt			(B)	Lithium sulphate
	(C)	Dipo	tassium	tartrate			Tungsten oxide
123.	RTD	(Resis	stance Te	emperatu	re Dete	ector) is an	
	(A)	activ	e transd	ucer		(D)	passive transducer
	(C)	indu	ctive tra	nsducer		(D)	capacitive transducer
124.	Very	small	resistan	ces can b	e meas	sured more acci	urately by
	(A)		stance be			(B)	Kelvin double bridge
	(C)	Ande	erson Br	idge		(D)	Schering bridge
125.	A br	idge ci	ircuit wo	orks at a	freque the br	ency of 2 kHz.	Which of the following can be used as a
	(A)	Head	dphones	and vibra	ation ga	alvanometers	
	DI	Head	dphones	and tuna	ble am	plifier	
	(C)	Vibr	ation gal	vanomet	er and	tunable amplif	ier
	(D)						unable amplifiers
CEE	E/18					24	
	12 30			10 10		12. 12. 13. 13. 13. 13. 13. 13. 13. 13. 13. 13	

121. Match:

- 126. A control system working under unknown random actions is called
 - (A) Computer control system
- (B) Digital data system
- (C) Stochastic control system
- (D) Adaptive control system
- 127. ______ technique gives quick transient and stability response.
 - (A) Root locus

(B) Bode


(C) Nyquist

- (D) Nichols
- 128. Phase margin of a system is used to specify
 - (A) frequency response

(B) absolute stability

relative stability

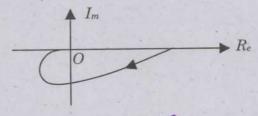- (D) time response
- 129. Pressure error can be measured by
 - Differential bellows and strain gauge
 - (B) Selsyn
 - (C) Strain gauge
 - (D) Strain gauge and potentiometer
- 130. An amplidyne can give which of the following characteristics?
 - (A) constant current
 - (B) constant voltage
 - (C) constant current and constant voltage
 - constant current, constant voltage and constant power
- 131. The polar plot of the system shown, the type of the system is




(A) 1

(3) 0

(C) 2

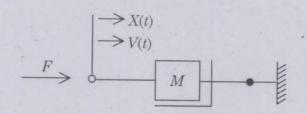(D) None of the above

The mass element can be expressed as 132.



(C) $F = \frac{Md^2x}{dt^2}$ (C) $F = K \int_{-\alpha}^{t} u \, dt$

If a step function is applied to the input of a system and the output remains below a certain level for all the time, the system is

- not necessarily stable
- (B) stable

unstable

(D) always unstable

134. The type 2 system has -- at the origin.

no net pole


(B) net pole

(C) simple pole two poles

The unit impulse response of a second order under damped system starting from the rest is 135. $c(t) = 12.5 e^{-6t} \sin 8t$, the steady state value of $t \ge 0$ unit step response of the system is equal to

- (A) 0
- (B) 0.25
- (C) 0.5

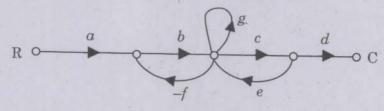136. The signal flow graph shown in figure, the value of C/R is



E							27		CEEE/18			
							0.7		CEEE/10			
	(C)	99					(D)	80				
	(A)	10					(3)	90				
141.				quirrel c		ductio	on motor r		10% is 100 kW, gross			
	(D)	Low r	esistan	ice and lo	w indi	uctan	ce					
	(0)			ice and h								
	(B)			nce and l	•							
	(A)			nce and l								
140.							ding shoul	d have				
	(A) (C)			uctance r	notor		Variable reluctance motor					
	(A)		ge mote		it com	inuo	(B)	Spherical motor				
139.							erating unus to run a	nloaded salient pole	synchronous motor			
	(D)	4	3	1	2							
	(C)	3	4	2	1							
	(B)	4	3	2	1							
	(4)	3	4	1 .	2							
		(a)	(b)	(c)	(d)							
	Code	es:										
	(a)	maucu	ion moi	.01		4.	Swindar	ne s test				
	(c) (d)	Alterna		ton		3. 4.		mpner's test				
	(b)	DC mo				2.		rotor test				
	(a)	Transfe				1.	Slip test					
		List I					List II					
138.	Mate		(Mach	ines) wit	h List	II (Te		lect the correct answer	r.			
	(C)	7200 1	rpm				(D)	1500 rpm				
	(A)	1800 1					0	3600 rpm				
137.				ed at which	ch the	neld	of alternat	or can be operated to	develop 60 Hz is			

142.	42. A single phase transformer when supplied from 220 V, 50 Hz has eddy current loss of 50 W If the transformer is connected to a voltage of 330 V, 50 Hz, the eddy current loss will be									
	(A)	168.75 W	OF	112.5 W						
	(C)	75 W	(D)	50 W						
143.	The	device which converts alternating o	current int	o direct current in a dc machine is						
	(A)	poles	(B)	brushes						
	(C)	armature winding		commutator						
144.	The 200 V		or of arma	ture resistance of 0.5Ω and back emf of						
	14	40 A	(B)	44 A						
	(C)	440 A	(D)	400 A						
145.	A DO		ected to sir	ngle phase AC supply. The torque produced						
	(A)	of zero average value								
	(B)	oscillating								
	(C)	steady and unidirectional								
	0	pulsating and unidirectional								
146.	A dy	namo has a rated armature curr	ent at 250 nplex wave	A. What is the current per path of the wound? The machine has 12 poles						
	(A)	250 A	(B)	125 A						
	(C)	20.833 A	(D)	10.4 A						
147.	are t	A power system consists of 300 buses out of which 20 buses are generator buses, 25 buses are the ones with reactive power support and 15 buses are the ones with fixed shunt capacitors. All the other buses are load buses. It is proposed to perform a load flow analysis using NR method. The size of NR Jacobian matrices								
	(A)	553 × 553	(B)	540 × 540						
	(C)	555 × 555	Dr	554 × 554						

- 148. A system is reactance grounded, if
 - $\frac{x_0}{x_1} > 3$ but less than that for resonant grounding
 - (B) $\frac{x_0}{x_1} > 3$
 - (C) $\frac{R_0}{x_1} > 3$
 - (D) $\frac{x_0}{x_1} > 3 \text{ and } \frac{R_0}{x_1} > 3$
- 149. The order of the lightning discharge current is
 - 10,000 amp

(B) 100 amp

(C) 1 amp

- (D) 1 micro-amp
- 150. A hydro-electric generating station is supplied from a reserviour of capacity 5×10^6 cubic metres at a head of 200 metres. The total energy available in kWh if the overall efficiency is 75% is
 - (A) $2.044 \times 10^6 \text{ kWh}$

(B) 252×10^6 kWh

(C) 775 kWh

- (D) 81620 kWh
- 151. The positive sequence component of voltage at the point of fault is zero when it is a
 - (A) 3-phase fault

(B) L-L fault

(C) L-L-G fault

- (D) L-G fault
- 152. The purpose of lead sheath in cables is
 - (A) to protect from mechanical wear and tear
 - to protect from moisture
 - (C) to give a round shape
 - (D) to provide a steel armour around it
- 153. Earth wire on EHV overhead transmission line is provided to protect the line against
 - lightning surge

- (B) switching surge
- (C) excessive fault voltages
- (D) corona effect

- 154. The number of flip flops required to construct a decade counter is
 - (A) 10

(B) 8

(6) 4


- (D) 3
- 155. Which one of the following is not correct?
 - (A) $P_i jQ_i = V_i^* \sum_{j=1}^n Y_{ij} V_j$
 - $V_i = |V_i|(\cos \delta_i + j\sin \delta_i)$
 - (C) Real power loss = $\sum_{i=1}^{n} P_i = \sum_{i=1}^{n} P_{gi} \sum_{i=1}^{n} P_{di}$ (Total generation) (Total load)
 - (D) $Q_i = \sum_{j=1}^{n} |Y_{ij}V_iV_j| \cos(\delta_i \delta_j \theta_{ij})$
- 156. A 132 kV transmission line has the weight of conductor = 680 kg/km; length of span= 260 m; ultimate strength = 3100 kg; safety factor = 2; and ground clearance = 10 m. The height above ground at which the conductor be supported is
 - (A) 10 m
 - (B) 3.7 m
 - (C) 260 m
 - (P) 13.7 m
- 157. The flip-flops belongs to a category of a logic circuits known as
 - (A) Monostable multivibrator
 - (B) Astable multivibrator
 - Bistable multivibrator
 - (D) One shot

- 158. In a common emitter configuration, calculate emitter current I_E in a transistor for which $\beta = 50$ and base current $I_B = 20$ μ A
 - (A) 0.102 mA

(B) 1.02 mA

(C) 10.2 mA

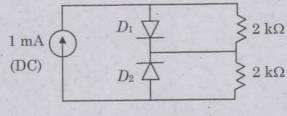- (D) 102 mA
- 159. Avalanche breakdown results due to
 - (A) process of rise in temperature
 - disrupting bonds
 - (C) strong electric field across the junction
 - (D) valance electrons
- 160. Assume the D1 and D2 in the figure are ideal diodes. The value of current I through D2 is



(A) 0 mA

(B) 0.5 mA

(C) 1 mA

- (D) 2 mA
- 161. If the ac input to a half wave rectifier has an r.m.s value of $400/\sqrt{2}$ volts, then diode PIV rating is
 - (A) $400/\sqrt{2} \text{ V}$

(B) $400 \times \sqrt{2} \text{ V}$

(6) 400 V

- (D) 202.84 V
- 162. The most desirable feature of a transformer coupling is
 - (A) higher voltage gain
 - (B) wide frequency range
 - ability to provide impedance matching between the stages
 - (D) ability to eliminate hum from the output

163. How many $32~\mathrm{K} \times 8~\mathrm{RAM}$ chips are needed to provide a memory capacity of $512~\mathrm{K}$ bytes?

(A) 32 chips

16 chips

(C) 8 chips

(D) 4 chips

164. For a full wave rectifier, match the following:

	Colu	mn A			Column I
(a)	I_{dc}			1.	0.482
(b)	Rippl	le factor		2.	$2I_m/\pi$
(c)	Effici	ency		3.	$I_m/\sqrt{2}$
(d)	$I_{\rm rms}$			4.	0.812
	(a)	(b)	(c)	(d)	
(A)	1	2	3	4	
P	2	1	4	3	
(C)	3	1	4	2	
(D)	4	9	1	0	

165. The a.c drain resistance of a JFET is calculated using

- $\frac{\Delta V_{DS}}{\Delta I_D}$ at constant V_{GS}
- (B) $\frac{\Delta I_D}{\Delta V_{GS}}$ at constant V_{DS}
- (C) $\frac{\Delta V_{GS}}{\Delta I_D}$ at constant V_{DS}
- (D) $\frac{\Delta I_D}{\Delta V_{DS}}$ at constant V_{GS}

166. The effect of source inductance on the performance of single phase and three phase full converter is to

- (A) reduce the ripples in the load current
- (B) make the discontinuous current as continuous
- reduces the output voltage
- (D) increases the load voltage

167. Resonant pulse inverters are used fo	167.	Resonant	pulse	inverters	are	used	for
-------------------------------------------------------------	------	----------	-------	-----------	-----	------	-----

- (A) Generating large peak voltage
- Overcoming the switching losses
- (C) Eliminating the harmonics
- (D) Converting a square wave into sine wave

168. A single phase half bridge inverter is feeding a load of 2.9 Ω from 48 V DC source. The RMS output voltage at fundamental frequency is

(A) $2 \times 48/\pi$

(B) $2 \times 48/\sqrt{2}\pi$

 $(\sqrt{2} \times 48)/\pi$

(D) $(2 \times 48)/2\sqrt{2}\pi$

169. The output voltage waveform of a three phase square-wave inverter contains

(A) only even harmonics

(B) both odd and even harmonics

only odd harmonics

(D) only triple harmonics

170. The number of junctions in a silicon controlled rectifier is

(A) two

(B) three

(C) four

(D) six

171. Which one of the following is not a current triggered device?

(A) SCR

(B) GTO

(C) TRIAC

MOSFET

172. Number of thyristors, each with the rating of 500 V, 75 A required in each branch of a series – parallel combination for a circuit with the total voltage and current rating of 7.5 KV and 1 KA respectively. If the device derating factor is 14%, then what is the number of thyristors in series and parallel branch respectively?

	No.of thyristor	No.of thyristors in parallel branch
(A)	18	16
(B)	15	14
(C)	12	12
(D)	16	18

173.	ADC	motor with the supply from singl	e phase ha	alf controlled rectifier can be operated in
	445	Forward motoring		
	(B)	Reverse motoring and reverse br	aking mod	le
	(C)	Forward motoring and forward b	oraking mo	ode
	(D)	Reverse motoring and forward b	raking mo	de
174.	Inas	single phase cyclo converter, an in	ter group 1	reactor is used to
	(A)	Reduce the current ripples		
	(B)	Reduce the voltage ripples		
	VOT	Limit the circulating current		
	(D)	Limit di/dt		
175.	overa		opper is fe	f rectangular pulse of duration 1 msec in ed by 100 V DC, then the average value of
	4	33.33, 1.41	(B)	66.66, 1.41
	(C)	33.33, 1	(D)	66.66, 1
176.		ost regulator has an input voltage	e of 5V an	d the average output voltage of 15 V. The
	(A)	3/2	(B)	2/3
	(C)	5/2	(D)	15/2
177.	The r	result of the instruction NEGCH in	1 8086 rest	ılts in
	(A)	CH one's complemented	(B)	CH two's complemented
	(C)	CH nine's complemented	(D)	CH ten's complemented
178.	The i	nstruction RST 7 is a		
	(A)	Restart instruction that begins th	he execution	on of a program
	45)	One-byte call to the memory add		
	(C)	One-byte call to the memory add		
	(D)	Hardware interrupt		
CEE	E/18		34	

- 179. Calculate the Full-scale output for an 8-bit DAC for the (0 to 10) Volt range
 - (A) 9.691 Volt . .

9.961 Volt

(C) 9.5 Volt.

- (D) 10 Volt
- 180. The average power of the energy signal is
 - (A) Finite

Zero

(C) Infinite

(D) Between 2 and 4

- 181. $\sin c(x)$ function is defined as
 - (A) $\sin c(x) = \frac{\pi x}{\sin(\pi x)}$

 $\sin c(x) = \frac{\sin(\pi x)}{\pi x}$

(C) $\sin c(x) = \frac{\sin \pi x}{\pi}$

- (D) $\sin c(x) = \frac{\pi}{\sin(\pi x)}$
- 182. The analog signal, $m(t) = 4\cos 100 \pi t + 8\sin 200 \pi t + \cos 300 \pi t$, the Nyquist sampling rate will be
 - (A) $\frac{1}{100}$ sec

(B) $\frac{1}{200}$ sec

 $\frac{1}{300}$ sec

- (D) $\frac{1}{600}$ sec
- 183. The ISR status of 8259 after IR4 is accepted is
 - (A) 7, 6, 5, 4, 3, 2, 1, 0

(B) 0, 7, 6, 5, 4, 3, 2, 1

2, 1, 0, 7, 6, 5, 4, 3

- (D) 3, 2, 1, 0, 7, 6, 5, 4
- 184. For latching the content of a counter of 8253 while the count is still going on
 - (A) The bits D7 and D6 of the control word are to be made 0
 - The bits D5 and D4 of the control word are to be made 0
 - (C) The bits D3 and D2 of the control word are to be made 0
 - (D) The bits D1 and D0 of the control word are to be made 0
- 185. No. of modes of operation in 8255A PPI is
 - (A) 1
- (B) 2
- 105 :
- (D) 4

186.		cells, each with an emf of 2 V and In-		
	(A)	$E = 2V$; $R_{\rm in} = 0.5 \Omega$	VB)	$E = 10V$; $R_{\rm in} = 2.5 \Omega$ $E = 10V$; $R_{\rm in} = 0.1 \Omega$
	(C)	$E = 2V$; $R_{in} = 0.1\Omega$	(D)	$E = 10V$; $R_{\rm in} = 0.1\Omega$
187.	Inaf	fuel cell the negative electrode is of		
	(A)	Carbon monoxide	(B)	Hydrogen
	(C)	Oxygen	(D)	Ammonia
188.	The p	process that converts solid coal in to lie	uid H	ydro carbon fuel is called
	W	Liquefaction	(B)	Carbonation
	(C)	Catalytic conversion	(D)	Hydrolysis
189.	The t	heoretical conversion efficiency of hyd	rogen -	oxygen fuel cell at 25° C is
	(A)	56% (B) 17%	(C)	75%

190. Super capacitor is a

(A) Generator

- Battery alone (B)
- Hybrid of capacitor and a battery
- (D) Motor

The tip speed ratio of the wind turbine is defined as

 $\lambda = \omega_r R$ (A)

 $\lambda = V/(\omega_r R)$ (C)

(D) $\lambda = (\omega_r R)/V$ $\lambda = \frac{V}{\omega_r}$

How many blades does a modern wind turbine have? 192.

- (A)
- (C) 4
- (D) 1

The wind intensity can be described by

Reynolds number

(B) Mach number

Beaufort number

(D) Froude number series

194.	In a PCM system a 5 bit encoder is used. Suppose each represents 1 Volt, what is the range of encoder?					
	(A)	0 - 32 V	(8)	0-31 V		
	(C)	1 – 31 V	(D)	$1-32~\mathrm{V}$		
195.		n a subroutine is called, the addres	s of the ir	nstructions following the CALL instruction		
	(A)	Stack Pointer	(B)	Accumulator		
	(C)	Program Counter	OF .	Stack		
196.	In P	V systems, 1 equivalent sun indicate	es a solar	irradiance of		
	W	1000 W/m ²	(B)	100 W/m ²		
	(C)	10 W/m ²	(D)	1 W/m²		
197.	at t given (A)	he junction of two media having by	ng relativ	the refracted angle θ_t of a light beam falling the refractive indices of n_1 and n_2 is $n_1 \sin \theta_i = n_2 \sin \theta_t$ $n_1 \cos \theta_i = n_2 \sin \theta_t$		
198.	The	voltage factor for a typical silicon ce	ll is			
	(A)	0.4	(8)	0.5		
	(C)	0.6	(D)	0.7		
199.	The	hour angle of solar radiation is				
	(A)	5° / hour	(B)	10° / hour		
	(0)	15° / hour	(D)	20° / hour		
200.	The	fill factor FF of a solar cell is define	d as			
	(A)	$V_{oc} \cdot I_{sc}$	(B)	$V_{oc} \cdot I_{sc} / P_{min}$		

(D) P_{max}/P_{min}

 $P_{max}/V_{oc} \cdot I_{SC}$

CEEE/18 [Turn over